

Implementation of T Flip-Flop using 7474 IC

Cheenepalli Chandana

September 22, 2022

1 Abstract

This manual shows Implementation of T flip-flop using 7474 IC

2 Components

Component	Value	Quantity
Bread board	-	1
Arduino	Uno	1
LED	-	2
IC	7474	1
Jumper Wires	-	20

Table 1:

3 Procedure

- 1.consider four digital pins 13,7,2,4,7 as input and 2,4 as ouputs .
- 2.here D13 acts as clock signal
- 3.connect 7474(1,4:VCC) to deactivate them otherwise they will interrupt in output
- 4.connect 7474(7:GND 14:VCC)
- 5.connect 7474(2:7,5:4) and take slider switch as toggle input connect it to D2.

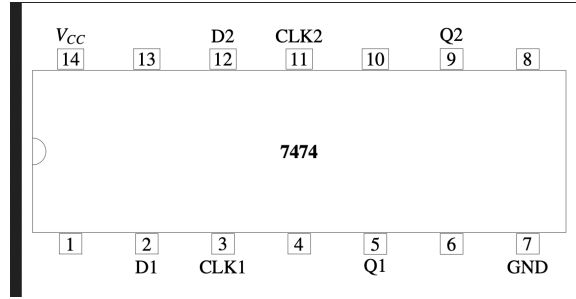


Figure 1: 7474

6. $D = T!Q$ — $!TQ$.

7. Connect another LED + to the 5 (Q) pin of the IC 7474 and GND the other terminal.

8. Change the D2 pin in the Arduino from VCC to GND and observe the outputs.

4 Code

Execute the following code using the below provided link

https://github.com/chandana531/cchandana_fw/blob/main/assignment1_assembly/codes/ide.ino

5 Conversion table

Input	Intermediate Inputs			Outputs	
T	Q_n	$!Q_n$	$T = D \text{ xor } Q_n$	Q_n	$!Q_n$
0	0	1	0	0	1
0	1	0	1	1	0
1	0	1	1	1	0
1	1	0	0	0	1

Table 2:

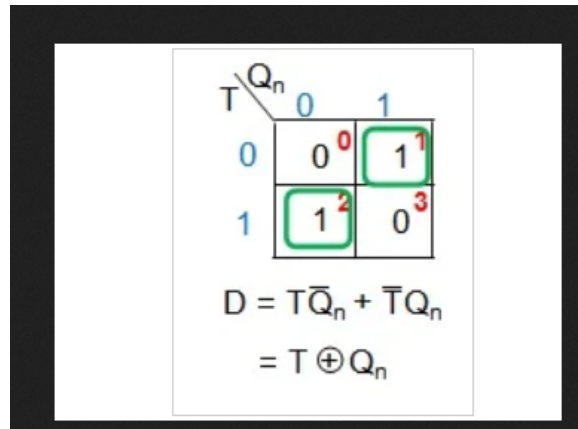


Figure 2: kmap

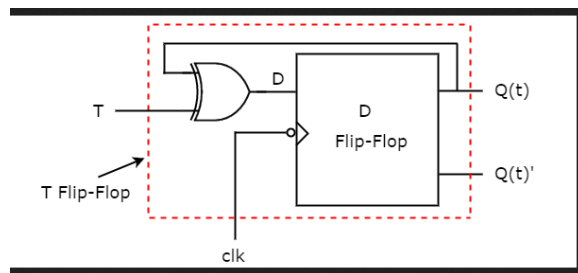


Figure 3: Circuit Diagram